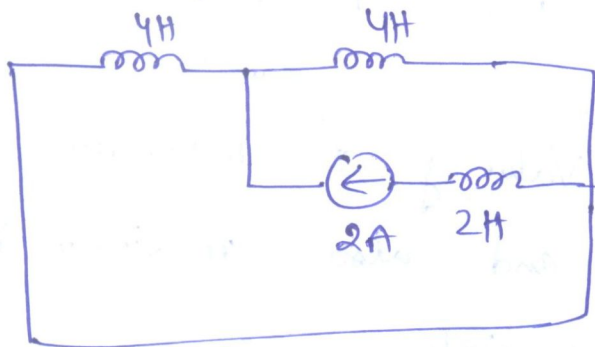



NETWORK THEORY

QUIZ

1. In the circuit given below, the flux linkages of the 2H inductor is _____




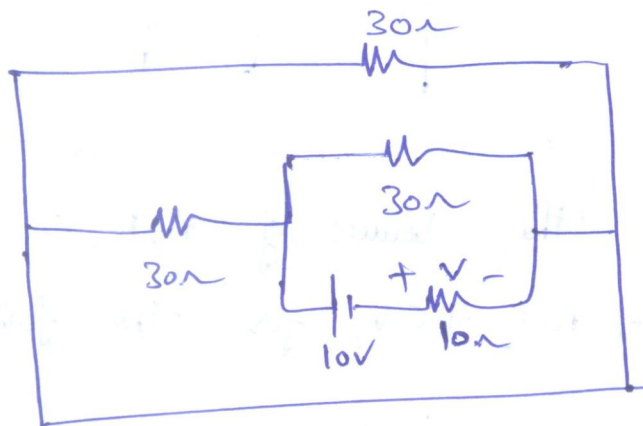2. The value of 'V' from the given below circuit is _____ Volts.




3. power dissipated in a bulb of 60W/230V. If we apply 200V across it is _____ Watts.

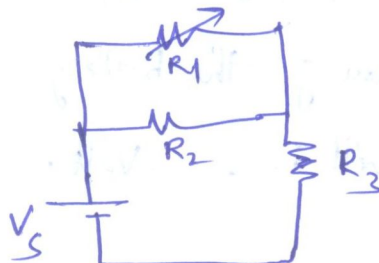
4. for what value of R_1 maximum power dissipation in R_2



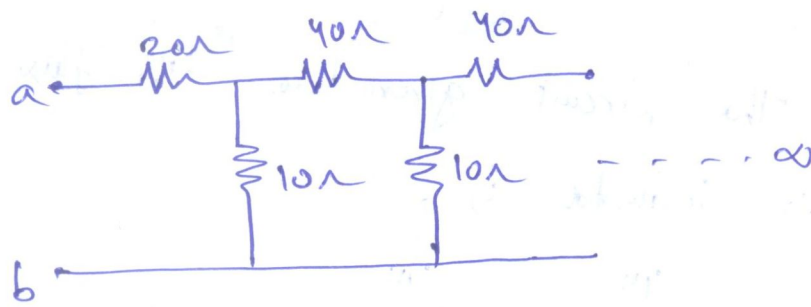
5. find equivalent resistance across terminal ab



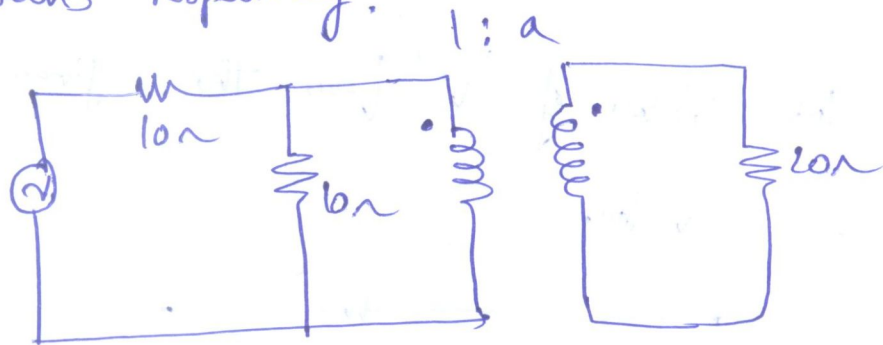
6. For what value of 'a' maximum power transferred to 20Ω and also maximum value of power in watts respectively.



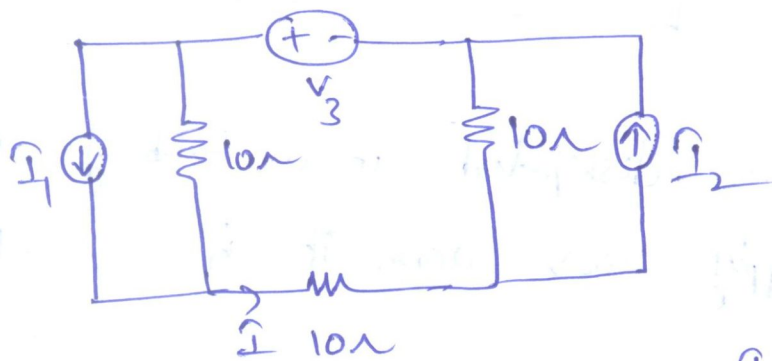7. Estimate the values of A, B, C. If I is defined as $A I_1 + B I_2 + C V_3$ for the following circuit.




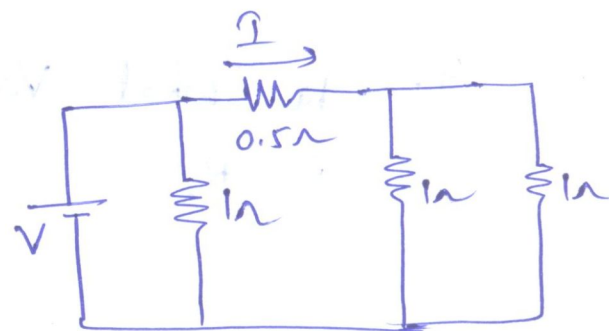8. In the circuit, if $I = 2A$, then the value of the battery voltage V will be _____ Volt.




9. If $i(t) = 4 + 3 \cos(10t - 30^\circ) + 4 \sin(10t + 30^\circ)$ is passing through resistor of 10Ω . power dissipated in 10Ω is _____ watts.

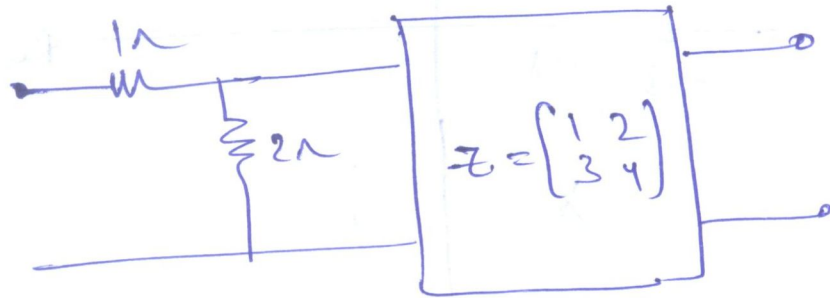
10. Consider the below circuit, determine Z_{12} of complete two port network



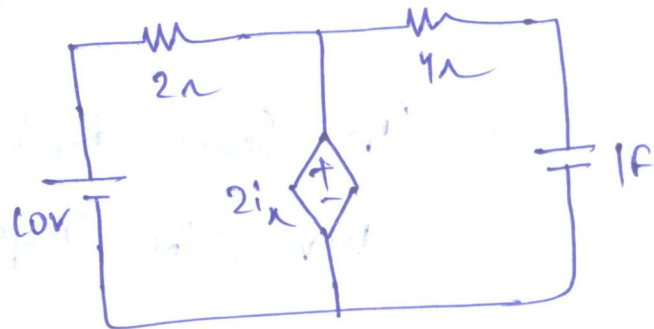
11. Consider below circuit, time constant (τ) of the circuit is _____ sec.



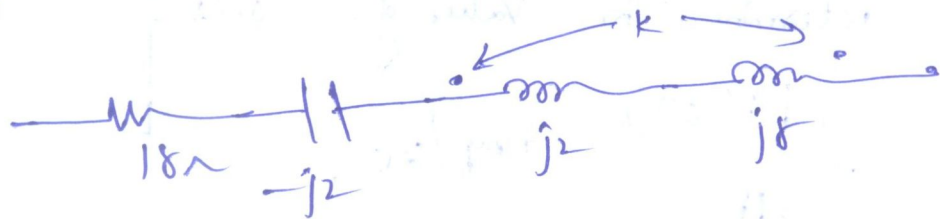12. for _____ value of 'k' the circuit is under magnet resonance? (k = coefficient of coupling)




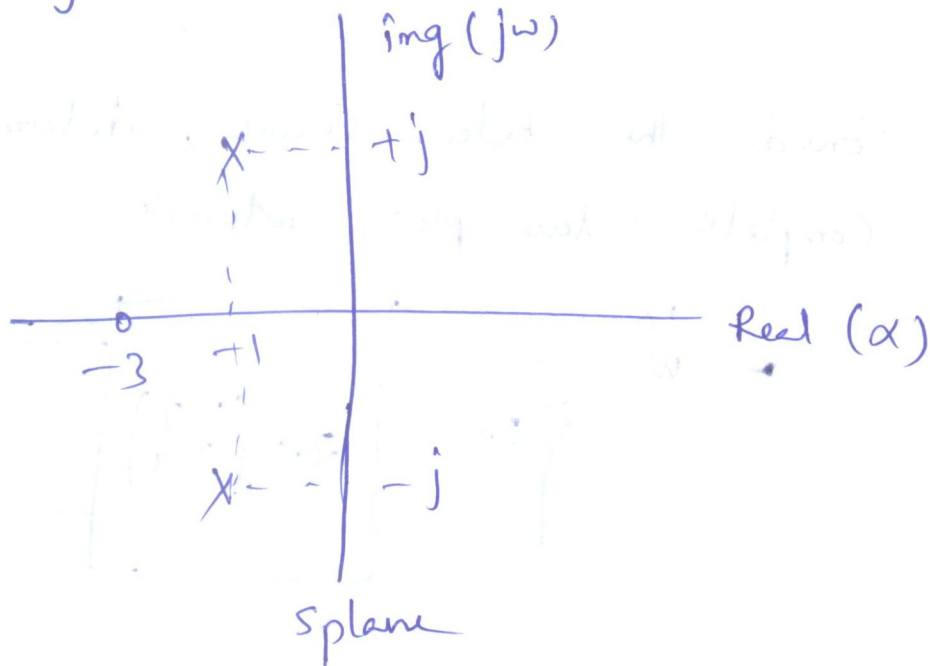13. The driving point impedance $Z(s)$ of a network has the pole zero locations as shown in fig. $Z(j0) = 3$, then $Z(s)$ is _____




14. In Series R, L, C Circuit with applied Voltage of 10V, the response $i(t) = 3e^{-2t} - 3e^{-4t}$ then values of R, L, C are _____, _____, _____.

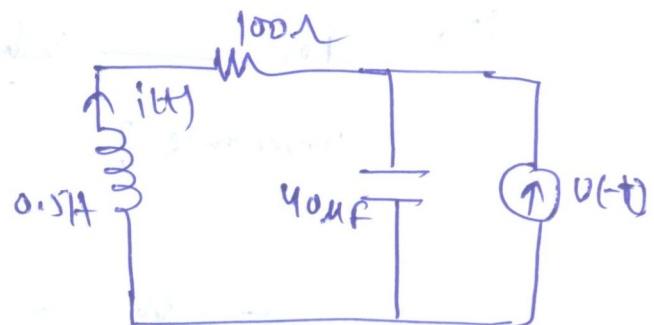15. Consider the figure, determine the value of $\frac{di(t)}{dt}$ Amp/sec.



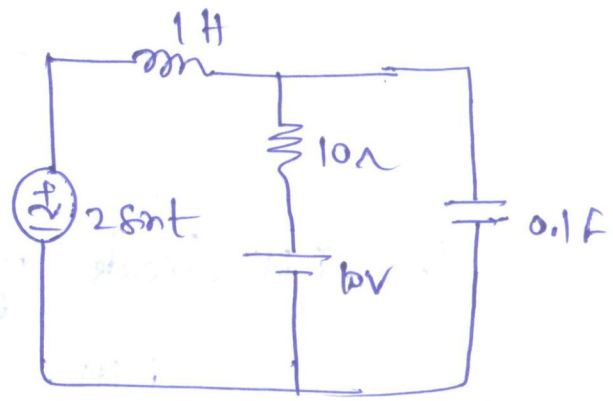5. power supplied by 10V source is _____ Watts.




[Faint handwritten notes and calculations are visible in the background, including the word 'inductor' and some mathematical expressions.]

4. Consider below figure,
 the value of 'V' by
 using data provided in
 figure-1 is _____ volts.



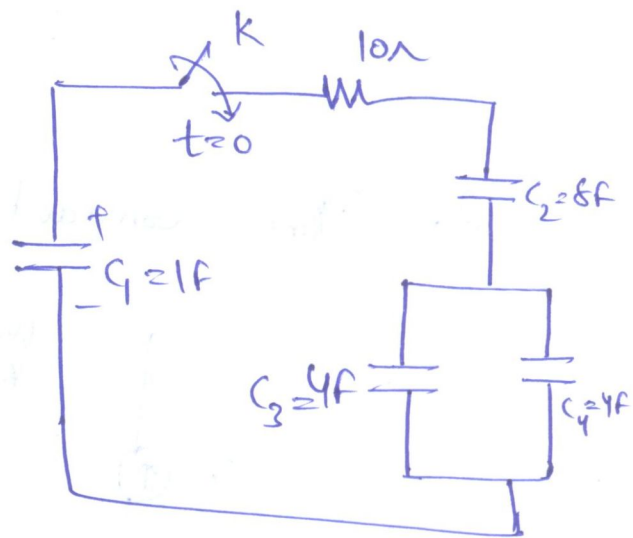
5. The steady state energy
 stored in C_2 is _____ joules
 (initial voltage across C_1 is
 10V)




NETWORK THEORY

ASSIGNMENT

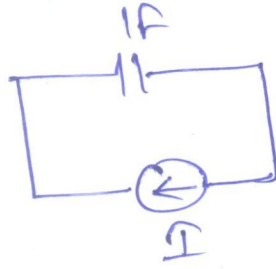1. If current flowing through the capacitor is $i(t+2) - i(t-2)$ then charge in capacitor at $t=0^+$ and energy in capacitor at $t=4$ sec respectively.



2. Time Constant of the circuit is _____

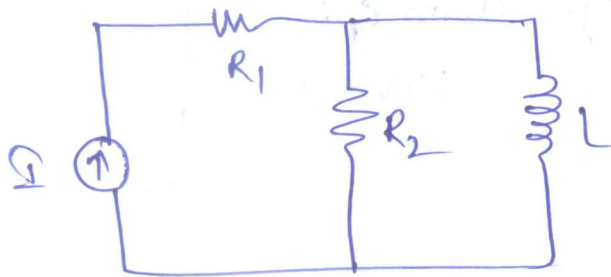

3. Identify the location of dots as shown in below figure

