 


**LINEAR IC'S & PULSES CIRCUITS LABORATORY  
MANUAL (EEE-318)  
(III/IV EEE I<sup>st</sup> Semester)**



**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING  
ANIL NEERUKONDA INSTITUTE OF TECHNOLOGY & SCIENCES**

(Affiliated to AU, Approved by AICTE & Accredited by NBA)  
SANGIVALASA-531 162, Bheemunipatnam Mandal, Visakhapatnam District  
Phone: 08933-225083/84/87 Fax : 226395

**Linear IC's and Pulse Circuit Laboratory**  
**III/IV EEE I<sup>st</sup> semester**  
**(CODE - EEE 318)**

DEPARTMENT OF  
ELECTRONICS & COMMUNICATION ENGINEERING



**LABORATORY MANUAL**

**Prepared By:**

**Mrs.P.S.M.Veena**  
Assistant Professor,  
Department of ECE.

**Approved By:**

**Dr.V.Rajya Lakshmi,**  
Professor & HOD,  
Department of ECE,ANITS

**ANIL NEERUKONDA INSTITUTE OF TECHNOLOGY & SCIENCES**  
**(Affiliated to Andhra University)**  
Sangivalasa-531162, Bheemunipatnam Mandal, Visakhapatnam.  
Phone:089335084,226395

## **INTRODUCTION**

In pulse circuits lab students will be able to analyze and design different linear and non-linear waveforms with different time constants and different types of inputs, with and without reference voltages using linear and non-linear wave shaping circuits. Design, analysis and voltage regulators circuits will be done.

In Integrated circuits lab Design and analysis of linear and non-linear circuits using operational amplifiers, 1st & 3<sup>rd</sup> order active filters, voltage regulators, multivibrators using timers, Schmitt trigger circuits will be done. Identification, verification and applications of ICs like LM741, 555 timer and three terminal regulators (7805, 7808 etc) will be taught. With this knowledge students will be able to do the mini-projects with the help of integrated circuits.

<b>LINEAR INTEGRATED CIRCUITS &amp; PULSE AND DIGITAL CIRCUITS LABORATORY</b>	
<b>EEE 318</b>	<b>Credits : 2</b>
<b>Instruction : 3 Periods / Week</b>	<b>Sessional Marks : 50</b>
<b>End Exam : 3 Hours</b>	<b>End Exam Marks : 50</b>

**Prerequisites:**

1. Pulse and Digital Circuits (EEE 313)
2. Linear IC's and Applications (EEE 314)

**Course Objectives:**

At the end of the course students should understand:

- To understand the linear and non-linear applications of operational amplifiers(741)
- To familiarize with theory and applications of 555 timers.
- To design and construct waveform generation circuits using Op-Amp
- Understand the response of linear circuits for different signals.
- Determine the voltage transfer characteristics of non linear circuits and also learn about comparators

- ~~Understand different energy resources~~
- ~~Electrical energy generation by using different types of plants.~~
- ~~Utilization of generated electrical energy for various purposes.~~
- ~~Electric heating, welding, illumination are known~~

**Course Outcomes:**

At the end of the course student should be able to:	
1.	Design the circuits using op-amps for various applications like adder, subtractor, integrator, differentiator and Schmitt trigger
2.	Design active filters for the given specifications and obtain their frequency response characteristics.
3.	Design and analyze multi vibrator circuits using op-amp, Transistor and 555Timer
4.	Design application based on linear and nonlinear circuits
5.	Understand the operation & application of Bootstrap circuit

**Mapping of course outcomes with program outcomes:**

CO	PO												PSO	
	1	2	3	4	5	6	7	8	9	10	11	12	1	2
1	1	1	3	3	1	1	0	0	2	1	0	0	1	0
2	1	1	3	1	1	1	0	0	2	1	0	0	1	0
3	1	1	3	2	1	1	0	0	2	1	0	0	1	0
4	1	1	3	3	1	1	0	0	2	1	0	0	1	0
5	1	1	3	1	1	1	0	0	2	1	0	0	1	0

- Formatted: Not Highlight
- Formatted: Indent: Hanging: 0.55"
- Formatted: Font: Not Bold, Not Highlight
- Formatted: Font: Not Bold, Not Highlight
- Formatted: List Paragraph, Indent: Left: 0.94", Hanging: 0.19", Don't add space between paragraphs of the same style, Line spacing: single, Outline numbered + Level: 4 + Numbering Style: 1, 2, 3, ... + Start at: 1 + Alignment: Left + Aligned at: 2.5" + Tab after: 3" + Indent at: 3", Tab stops: Not at 3"
- Formatted: Font: Not Bold, Not Highlight
- Formatted: Not Highlight
- Formatted: Indent: Hanging: 0.49"
- Formatted: Indent: Left: 0.31", Hanging: 0.19"
- Formatted: Not Highlight

Formatted: Font: Bold, Not Highlight

- Formatted: Not Highlight
- Formatted: Not Highlight

|  
|  
|

~~TEN EXPERIMENTS BASED ON EEE 313 & EEE 314 SYLLABI~~

Formatted: Normal, No bullets or numbering

## **Linear IC's and Pulse Circuit Laboratory**

**III/IV EEE 1<sup>st</sup> semester**

**(CODE - EEE 318)**

### **List of Experiments**

	<b>Page No.</b>
1. Applications Of Operational Amplifier	6
2. Linear Wave Shaping	13
Non- Linear Wave Shaping	
3. Clipper Circuits	17
4. Clamper Circuits	22
5. Schmitt Trigger	25
6. IC Voltage Regulator	30
7. UJT As A Relaxation Oscillator	34
8. Astable Multivibrator Using 555 Timers	37
9. Bistable Multivibrator	41
10. Frequency Response Of A Active Filter	44
11. IC Op-Amp Boot-Strap Ramp Generator	48

**EXPERIMENT NO: 1**  
**APPLICATIONS OF OPERATIONAL AMPLIFIER**

**AIM :** To realize Summing Amplifier, Subtracting Amplifier, Integrator and Differentiator by using 741 Op-Amp.

**APPARATUS:**

1. Op-Amp LM 741
2. Resistors – 1K $\Omega$  (4), 100K $\Omega$  (1), 10K $\Omega$  (1)
3. Capacitors – 0.01 $\mu$ f(1), 330pf(1)
4. Function Generator
5. TRPS
6. CRO & CRO Probes
7. Bread Board
8. Connecting Wires.

**THE IDEAL OP AMP:**

An ideal op amp would exhibit the following electrical characteristics.

1. Infinite voltage gain A.
2. Infinite input resistance  $R_i$  so that almost any signal source can drive it and there is no loading of the preceding stage.
3. Zero output resistance  $R_o$  so that output can drive an infinite number of other devices.
4. Zero output voltage when input voltage is zero.
5. Infinite bandwidth so that any frequency signal from 0 to  $\infty$  Hz can be amplified without attenuation.
6. Infinite common mode rejection ratio so that output common – mode noise voltage is zero.
7. Infinite slew rate so that output voltage changes occur simultaneously with input voltage changes.

**APPLICATIONS OF OP AMP:**

**1. Summing Amplifier:**

Op amp may be used to design a circuit whose output is the sum of several input signals. Such a circuit is called a summing amplifier or a summer. If  $V_1$ ,  $V_2$  are two input signals given to the inverting terminal, then

$$V_o = - \frac{R_f}{R} (V_1 + V_2)$$

2. **Subtracting Amplifier:**

The function of a subtractor is to provide an output, which is equal to the difference of two input signals (or) proportional to the difference of two input signals. If  $V_1$  and  $V_2$  are the input voltages at inverting and non – inverting terminals, then

$$V_o = \frac{-R_f}{R} (V_1 - V_2)$$

3. **Integrator:**

A circuit in which the output voltage waveform is the integral of the input voltage waveform is the integrator or the integration amplifier. Such a circuit is obtained by using a basic inverting amplifier configuration with the feedback resistor  $R_f$  replaced by a capacitor  $C_f$ . The output voltage is given by

$$V_o = - \frac{1}{RC} \int V_1 dt$$

Integrator is used in signal wave shaping circuits and in analog computers. If the input is a sine wave, the output is a cosine wave. If the input is a square wave, the output will be a triangular wave. In the practical integrator,  $R_f$  is connected across feedback capacitors  $C_f$ . This  $R_f$  limits the low frequency gain and minimizes the variation in the output voltage. The input signal will be integrated properly if the time constant

$$T = R_1 C_f \text{ is larger than the time period } T \text{ of the input signal}$$

4. **Differentiator:**


The function of a differentiator is to give an output voltage, which is proportional to the rate of change of input voltage. The differentiator may be constructed from a basic inverting amplifier if an input resistor is replaced by capacitor  $C_1$ . The output voltage is given by

$$V_o = - RC (dV_i / dt)$$

The condition for differentiator is  $\omega \ll T$  where  $\omega = \frac{1}{RC}$  for sine wave and square wave inputs, the resulting differentiated outputs are cosine wave and spike outputs respectively. Differentiator is used to detect high frequency components in an input signal.




 **CIRCUIT DIAGRAM: (i) Summing Amplifier**



$R_1=R_2=R_3=R_f = 1K\Omega$


**(ii) Subtracting Amplifier**

 

$R_1=R_2=R_3=R_4=1K\Omega$

 
**(iii) Differentiator:**

$R_1=1K\Omega, R_2=100K\Omega ; C_1=0.01\mu f, C_f=330pf ; V_{in} = 0.4v$  peak to peak at 1kHz


 
#### (iv) Integrator:

$R=10K\Omega$ ,  $R_f=100K\Omega$ ,  $C=0.01\mu f$ ,  $V_s = 4v$  peak to peak at 10kHz



#### PROCEDURE:

##### I. Summing Amplifier:

1. Connections are made as per the circuit diagram.
2. Input voltages  $V_1$  and  $V_2$  are given and the corresponding output voltage  $V_o$  is measured from CRO.
3. Output varies as  $V_o = -(V_1 + V_2)$ , since  $R_f = R$ .

##### II. Subtracting Amplifier:

1. Connections are made as per the circuit diagram.
2. Input voltage  $V_1$  and  $V_2$  are given to the inverting and non – inverting terminals respectively and corresponding output voltage is measured from CRO.
3. Output varies as  $V_o = V_2 - V_1$ .



##### III Differentiator:

1. Connections are made as per the circuit diagram.
2. A square wave input of 4V (p-p) and frequency of 1KHZ is applied from function generator.
3. Output waveform is observed. Corresponding amplitude and time period is observed and frequency is calculated.
4. With the above data plot the output graphs with time on X-axis and voltage on Y-axis.

##### IV. Integrator:

1. Connections are made as per the circuit diagram.
2. By using a function generator, a square wave input 4Vp-p is given.
3. The frequency applied is 10 KHz.
4. A perfect triangular wave is obtained. The peak-to-peak voltage and the time period of input and output waves are measured from CRO.
5. The waveforms are plotted.

**MODEL GRAPHS:  
INTEGRATOR:**

  

DIFFERENTIATOR:


 


Fig. Input and Output waveforms for Square wave

 

**PRECAUTIONS:**

1. Loose and wrong connections are to be avoided.
2. Waveforms should be obtained without any distortion.

**Conclusion:****RESULT:****Viva questions**

1. What are the ideal characteristics of an OP-AMP?
2. Define OP-AMP.
3. What do you mean by CMRR?
4. Define slew rate.
5. What are the applications of differentiator?
6. What are the applications of integrator?
7. What is a difference between inverting and non-inverting amplifier?

**EXPERIMENT NO: 2**  
**LINEAR WAVE SHAPPING**


**AIM:** To observe the process of linear wave shaping for square wave input for high pass RC circuit and low pass RC circuit.

**APPARATUS:**


1. Resistors – 1KΩ (1) & 10KΩ (1)
2. Capacitors – 1μf(1) & 0.01μf(1)
3. Function Generator
4. TRPS
5. CRO & CRO probes
6. Bread Board and connecting wires.

**CIRCUIT DIAGRAM:**

High Pass RC Circuit

 

Low Pass RC Circuit

 

**High pass RC Circuit:**

The reactance of a capacitor decreases with increasing frequency; the higher frequency components in input signal appear at the output with less attenuation than do the lower frequency components. At very high frequency the capacitor acts almost as a short circuit and virtually all the input appears at the output. This is behavior accounts for the designation 'High Pass Filter'.

Square wave responses of a high pass RC circuit.

The dashed curve represents the output if  $RC \gg T$ .

$$V_1^1 = V_1 \exp(-T_1/RC) \quad V_1^1 - V_2 = V$$

$$V_2^1 = V_2 \exp(-T_2/RC) \quad V_1 - V_2^1 = V$$

A symmetrical square wave is one for which  $T_1 = T_2 = T/2$ . Because of symmetry  $V_1 = -V_2$  and  $V_1^1 = -V_2^1$

$$V_1 = V / (1 + \exp^{-T/2RC})$$

$$V_1^1 = V / (1 + \exp^{T/2RC})$$

Peaking of square wave resulting from a time constant small compared with T.

The high pass RC circuit acts as a differentiator if time constant is very small in comparisons with the time required for the input signal to make an appreciable change.

#### Low Pass R-C Circuit:

The low pass RC circuit passes low frequencies readily but attenuates high frequencies because the reactance of capacitor decreases with increasing frequency. At high frequencies, the capacitor acts as a virtual short circuit and output falls to zero.

Square wave input (b-d) , output of low pass RC circuit. The time constant is smallest for (b) and largest for (d).

Equation of rising portion

$$V_{01} = V^1 + (V_1 - V^1) \exp^{-(t/RC)}$$

$V_1$  = initial value of output voltage .

Equation of falling portion

$$V_{02} = V^{11} + (V_2 - V^{11}) \exp^{-(t-T_1)/RC}$$

The low pass RC circuit acts as an integrator if time constant is very large in comparison with time required for the input signal to make an appreciable change.

#### PROCEDURE:

1. Connections are made as per the circuit diagram.
2. To the high pass circuit a square wave input of amplitude 10V (p-p) is given.
3. The time period of waveform is adjusted such that  $RC \ll T$ ,  $RC = T$  and  $RC \gg T$  to get spikes and tilted output respectively. The time period and amplitude are noted.
4. Now to the low pass circuit a square wave input of amplitude 10V (p-p) is given.
5. The time period of input signal is adjusted with the help of a function generator such that  $RC \ll T$  and  $RC \gg T$  to get the corresponding waveforms. The time period and amplitude are noted.
6. Graphs are plotted for both input and output waveforms of both the circuits when  $RC \ll T$  and  $RC \gg T$ .

**Observation Table:**


	High Pass RC Circuit									
	$RC \ll T$		$RC = T$				$RC \gg T$			
	$V_1$	$V_2$	$V_1$	$V_2$	$V'_1$	$V'_2$	$V_1$	$V_2$	$V'_1$	$V'_2$
Theoretical Calculations										
Practical Calculations										

	Low Pass RC Circuit					
	$RC \ll T$		$RC = T$		$RC \gg T$	
	$V_1$	$V_2$	$V_1$	$V_2$	$V_1$	$V_2$
Theoretical Calculations						
Practical Calculations						




**MODEL GRAPHS:**

**High pass circuit**

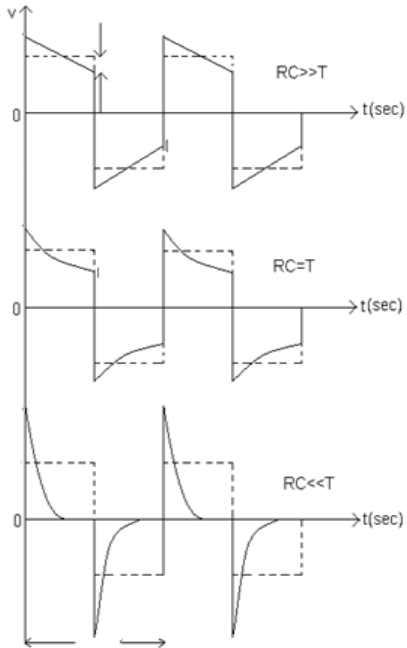

**Low Pass Circuit**

 

**PRECAUTIONS:**

1. Loose and wrong connections are to be avoided.
2. The output waveforms should be obtained without and distortion
3. Parallax error should be avoided.

**Conclusion:**

**RESULT:**

**Viva questions**

1. What is linear wave shaping?
2. How low pass RC circuit works as an integrator?
3. How low pass RC circuit works as differentiator?
4. Define time constant.
5. Define tilt.
6. Explain the output wave forms of high pass and low pass circuit for different conditions.

**EXPERIMENT NO:3**  
**CLIPPER CIRCUITS**

**AIM:**

To observe the waveforms of clipper circuits using

- a. Positive clipper
- b. Negative clipper
- c. Two level clipper or slicer circuit.


**APPARATUS:**

1. 1N 4007 diodes (2)
2. Resistor-10K (1)
3. TRPS
4. Function Generator
5. Bread board and connecting wires
6. CRO with CRO probes.

**CIRCUIT DIAGRAM:**


**Shunt Clippers Negative clipper:**

$R = 10K\Omega$

 

**Biased Shunt Positive Clipper**

Series Clippers :  $R_1=10K\Omega$

 

Biased series negative clipper


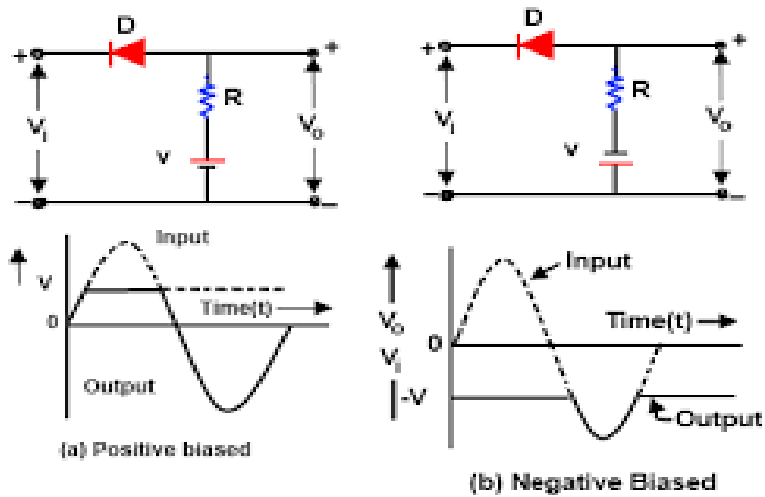


Figure 2: Series positive clipper with bias

**Two level clipper:  $R_1=10K\Omega$**

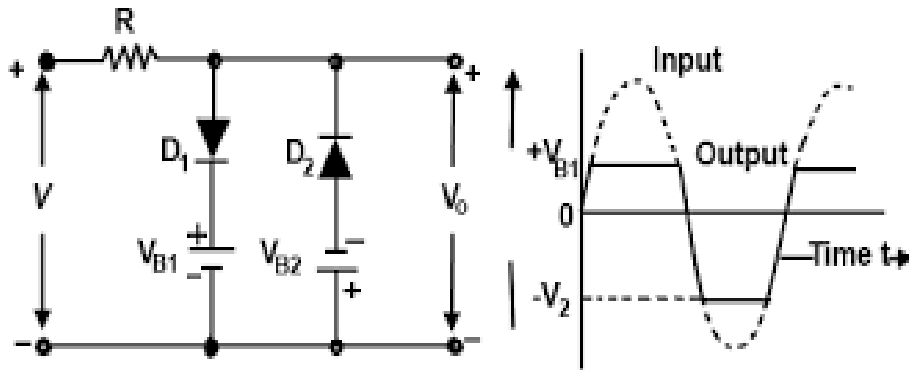

**Dual (Combination) Diode Clipper**

**CIRCUIT OPERATION:**

Clippers are used to select a part of signal waveform above or below a reference voltage for transmission.

**Negative Clipper:**

For  $V_i < V_R + V_r$ , The diode D is OFF, since it is reverse biased and hence does not conduct. Since no current flows, there is no voltage drop across R.

$$V_o = V_i \text{ for } V_i < V_R + V_r$$

Where  $V_r$  is Cut-in voltage of the diode.

For  $V_i > V_R + V_r$ , the diode D is ON, Since it is forward biased and the potential barrier is overcome

$$V_o = V_R + V_r$$

**Transfer characteristic Equation:**

$$V_o = V_i \text{ for } V_i < V_R + V_r$$

$$V_o = V_R + V_r \text{ for } V_i > V_R + V_r$$

**Positive Clipper:**

When  $V_i > V_R + V_r$  the diode is forward biased and hence it conducts since it is ON it is short circuited. It is obvious that  $V_o = V_R + V_r$  Whatever the comment.

When  $V_i < V_R + V_f$  the diode is reverse biased and hence it is OFF. It acts as an open circuit.  $V_o = V_i$

**Transfer Characteristic Equation:**

$$V_o = V_i \text{ for } V_i < V_R + V_f$$

$$V_o = V_R + V_f \text{ for } V_i > V_R + V_f$$

**Procedure:**

1. Connections are made as per the circuit diagram
2. For the positive clipper the diode is connected along with reference voltage as shown by applying the input and the output is observed on the C.R.O.
3. For the negative clipper the directions of diode and the reference voltage are reversed and by giving the input, the output is observed on the C.R.O.
4. For the Slicer Circuit has two Diodes along with reference voltages are connected as shown and output is observed on the C.R.O.
5. A sinusoidal input 10V (p-p) 1KHZ is given to positive clipper, negative clipper and slicer circuit and corresponding output is observed.

**OBSERVATIONS:**

Name Of the Clipper	Negative Clipper O/P		Output waveform
Wave Form	Positive peak	Negative peak	
Amplitude (p-p)			
Time Period			
Name Of the Clipper	Positive Clipper O/P		
Wave Form	Positive peak	Negative peak	
Amplitude (p-p)			
Time Period			

Name Of the Clipper	2-Level Clipper O/P		Output waveform
Wave Form	Positive peak	Negative peak	
Amplitude (p-p)			
Time Period			

**PRECAUTIONS:**

1. Loose and wrong connections are to be avoided.
2. The output waveforms should be obtained without distortion.
3. Parallax error should be avoided

**Conclusion:**

**RESULT:**

**Viva questions.**

1. What is meant by non linear wave shaping?
2. What is clipper? What are the different types of clippers?
3. What are the different applications of clipper?
4. What is two level clipper
5. Explain the operation of positive and negative clipper?

**EXPERIMENT NO:4**  
**CLAMPER CIRCUITS**

**AIM:**


To observe the waveforms of the Positive and Negative clamping circuits.

**APPARATUS:**

- 1) Capacitor 4.7 $\mu$ f - 1
- 2) 1N4007 diode - 1
- 3) Resistor 1M  $\Omega$  - 1
- 4) Function Generator
- 5) Bread board
- 6) CRO and CRO probes
- 7) Connecting wires.


**Circuit Diagrams:**

Negative Clamper

 

**C=4.7 $\mu$ f , R=1M  $\Omega$**


Positive Clamper

 

**C=4.7 $\mu$ f, R=1M  $\Omega$**

**Model Graph:**

 **POSITIVE CLAMPING AND NEGATIVE CLAMPING**



**PROCEDURE:**

1. The circuits are connected as per the circuit diagram.
2. The input signal  $V_i$  of (10V p-p) frequency (1KHz) is applied to each of the circuits.
3. The corresponding output waveforms are noted from the C.R.O.
4. The input and output waveform are plotted on the graph sheets.

**OBSERVATIONS:**

Name Of the Clamper	Negative Clamper O/P		Output waveform
	Positive peak	Negative peak	
Wave Form			
Amplitude (p-p)			
Time Period			



Name Of the Clamper	Positive Clamper O/P		Output waveform
	Positive peak	Negative peak	
Wave Form			
Amplitude (p-p)			
Time Period			

**PRECAUTIONS:**

1. Loose and wrong connections are to be avoided.
2. The output waveforms should be obtained without and distortion.
3. Parallax error should be avoided

**Conclusion:**

**RESULT:**

**Viva questions**

1. What do mean by clamper?
2. What are the different types of clamping circuits?
3. What are the different applications of clampers?
4. Why clamper is called DC inserter?
5. Explain the operation of positive clamper and negative clamper?

**EXPERIMENT NO: 5**  
**SCHMITT TRIGGER**

**AIM:**

To observe the output waveform of a Schmitt trigger circuit and to note down the hysteresis voltage  $V_{HY}$  with the reference of  $V_{UT}$  and  $V_{LT}$ .

**Apparatus:**

- 1) IC 741 OP-AMP -1NO
- 2) Resistors 2.2K $\Omega$  -2, 10k $\Omega$  -1
- 3) Function Generator
- 4) TRPS
- 5) CRO, Bread Board and connecting wires.

**Theory:**

The circuit shown is known as the Schmitt trigger or Squaring Circuit. It shows an working comparator with positive feedback. This circuit converts an irregular shaped waveform to a square wave hence it is called as a square wave generator.

If positive feedback is added to a basic comparator circuit, Gain can be increased greatly.

The input voltage  $V_{in}$  triggers the output  $V_o$  every time it exceeds certain voltage levels called upper threshold voltage  $V_{UT}$  and lower threshold voltage  $V_{LT}$

The threshold voltages are obtained by using the voltage divider  $R_1 - R_2$  where the voltage across  $R_1$  is fed back to the (+) input. The voltage across  $R_1$  is variable reference threshold voltage that depends on the value the polarity of the output voltage  $V_o$ . When  $V_o = +V_{SAT}$  the voltage across  $R_1$  is called the upper threshold Voltage  $V_{UT}$

The input voltage  $V_{IN}$  must be slightly more positive than  $V_{UT}$  in order to cause the output  $V_o$  to switch from  $+V_{SAT}$  to  $-V_{SAT}$  as long as  $V_{IN} < V_{UT}$ ,  $V_o$  is at  $+V_{SAT}$

$$V_{UT} = \frac{R_1}{R_1+R_2} (+V_{SAT})$$


$$V_{LT} = \frac{R_1}{R_1+R_2} (-V_{SAT})$$

The hysteresis voltage is equal to difference between  $V_{UT}$  and  $V_{LT}$

$$V_{HY} = V_{UT} - V_{LT}$$


$$V_{HY} = \frac{R_1}{R_1+R_2}(+V_{SAT}) - \frac{R_1}{R_1+R_2}(-V_{SAT})$$

**Pin Diagram:**

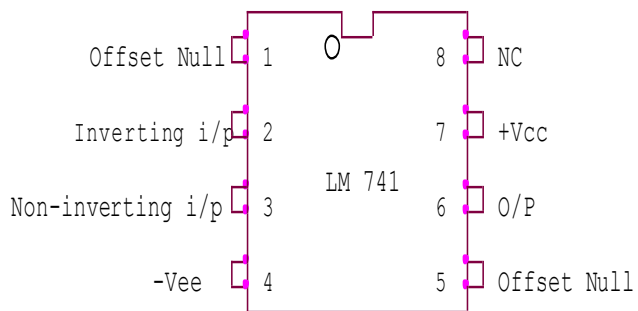

**Circuit Diagram:**


Schmitt Trigger

 

**R1=10KΩ, R2=R3=2.2KΩ**


**MODEL GRAPHS:**

 **Input and output waveform of Schmitt trigger:**



 **$V_0$  versus  $V_{in}$  plot of hysteresis voltage:**

**SCHMITT TRIGGER - INPUT OUTPUT CHARACTERISTICS-  
HYSTERESIS VOLTAGE PLOT**



**PROCEDURE:**

1. The circuit for Schmitt trigger is connected as per the given circuit diagram.
2. A sinusoidal input of 1 KHz is applied with the help of function generator.
3. A square wave output is obtained for the corresponding input for which the positive peak voltage (+Vsat) and negative peak voltage (-Vsat) are noted.
4. The upper threshold voltage (V<sub>UT</sub>) and lower threshold voltage (V<sub>LT</sub>) are calculated for the corresponding output.

5. The shift angle (θ) is calculated using the formula

$$V_{UT} = V_p \sin\theta$$

$$\sin\theta = V_{UT} / V_p$$

$$\theta = \sin^{-1} (V_{UT} / V_p )$$

6. The hysteresis voltage (V<sub>H</sub>) is calculated using the formula

$$V_{HY} = V_{UT} - V_{LT}$$

**Observations:**

**Input applied:** V<sub>i</sub> (p-p mV) =

F =

T =

**Output obtained:** +Vsat =

-Vsat =

T =

F =

**Calculations:**

**Upper threshold voltage:**

$$V_{UT} = \frac{R_1}{R_1 + R_2} (+V_{SAT})$$

**Lower threshold voltage:**

$$V_{LT} = \frac{R_1}{R_1 + R_2} (-V_{SAT})$$

**Hysteresis voltage** V<sub>HY</sub> = V<sub>UT</sub> - V<sub>LT</sub>

**Shift angle** θ = Sin<sup>-1</sup> (V<sub>UT</sub> / V<sub>p</sub>)

**Tabular Form:**

		<b>Amplitude</b>	<b>Time period</b>
<b>Input applied</b>	<b><math>V_i</math> (p-p) =</b>		
<b>output applied</b>	<b>+<math>V_{sat}</math>=</b>		
	<b>-<math>V_{sat}</math> =</b>		

**PRECAUTIONS:**

1. Loose and wrong connections are to be avoided.
2. The output waveforms should be obtained without and distortion.
3. Parallax error should be avoided.

**Conclusion:**

**RESULT:**

**Viva questions**

1. What do mean by Schmitt trigger?
2. What are the different applications Schmitt triggers?
3. What is meant by Hysteresis voltage?
4. What is meant by threshold voltage?

**EXPERIMENT: 6**  
**IC VOLTAGE REGULATOR**

**Aim:**

To obtain the voltage regulation of a 3-terminal fixed IC voltage regulator.

**Apparatus:**

- 1) IC 7808
- 2) Capacitor  $1\mu\text{F}$ ,  $0.1\mu\text{F}$
- 3) Voltmeter (0-10) V
- 4) Ammeter (0-100) mA
- 5) Decade resistance box (DRB)
- 6) TRPS
- 7) Bread board
- 8) Connecting wires.

**Theory:**


A voltage regulator is an electronic device that provides a stable dc voltage independent of load current, temperature and a.c voltage variations. Figure shows a regulated power supply using discrete components. The circuit consists of following parts.

1. Reference voltage circuit
2. Error amplifier
3. Series pass transistor
4. Feedback network.

It can be seen from the figure that the power transistor Q1 is in series with the un-regulated dc voltage  $V_{in}$  and the regulated output voltage  $V_o$  so it must absorb the difference between these two voltages whenever any fluctuation in output voltage  $V_o$  occurs

The transistor Q1 is also connected as an emitter follower and therefore provides sufficient current gain to drive the load. The output voltage is sampled by R1-R2 divider and feedback to the negative input terminal of op-amp error amplifier sample the output voltage. This sampled voltage is compared with the reference voltage  $V_{ref}$ . The output voltage  $V_o'$  of the error amplifier drives the transistor Q1.

**Internal Diagram:**

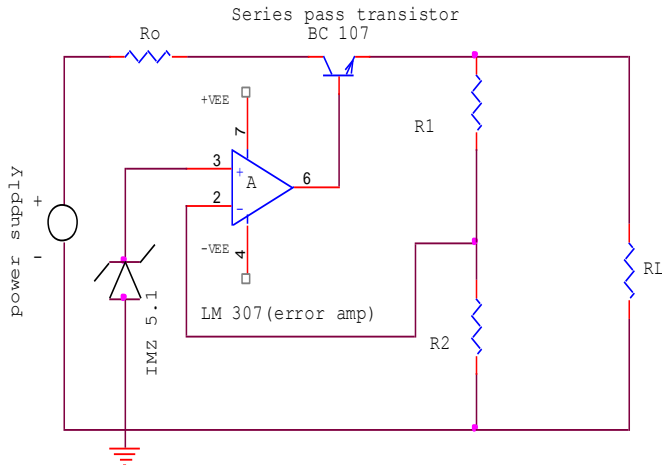


78XX series are three terminal positive fixed voltage regulators. There are seven voltage options available such as 5, 6, 8,12,15,18 and 24V. In 78XX series the last two numbers indicate the output voltage. For example 7808 indicates 8V regulator.

79 series are also 3-terminal IC regulator with fixed output negative voltage regulator.

In the standard representation of monolithic voltage regulator a capacitor 'C' is usually connected between input terminal and ground to cancel the inductive effect due to long distribution leads.


**CIRCUIT DIAGRAM:**

3-Terminal Fixed Voltage Regulator

 

$C1 = 1\mu F$  ,  $C2 = 0.1\mu F$



 

**Procedure:**

1. Connections are made as per the circuit diagram.
2. By adjusting the Voltage across RPS to 12V, the load terminals open circuited, the voltmeter reading is noted. This gives the no load voltage.
3. The load is varied from 10KΩ to 50Ω with the help of decade resistance box the corresponding voltmeter and ammeter reading are noted.
4. A graph is drawn between % voltage regulation on y-axis and load resistance on x-axis.


% voltage Regulation =

$$\frac{V_{NL} - V_L}{V_L} \times 100$$

**Tabular form**  $V_{NL} =$

$R_L (\Omega)$	I (mA)	V (Volts)	% Regulation
10KΩ			
to			
100Ω			

**Model Graph:**  
% Regulation

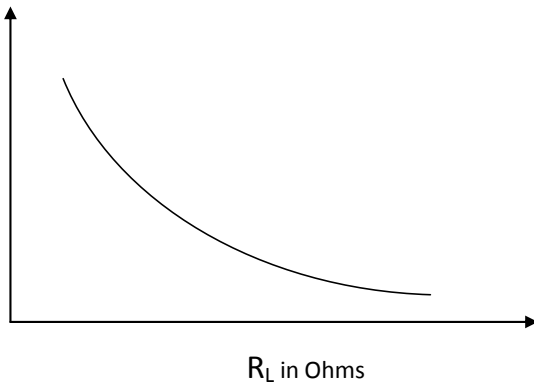

**PRECAUTIONS:**

1. Loose and wrong connections are to be avoided.
2. The output waveforms should be obtained without and distortion.
3. Parallax error should be avoided

**Conclusion:**

**RESULT:**

**Viva questions**

1. What do mean by voltage regulator?
2. What is error amplitude?
3. What is meant by error amplitude?
4. What is meant by threshold voltage?

**EXPERIMENT: 7**  
**UJT AS A RELAXATION OSCILLATOR**

**AIM:**

To obtain a saw tooth waveform using UJT and test its performance as an oscillator

**APPARATUS:**

- |  |     |
|--|-----|
| 1) UJT-2N 2646                                 | - 1 |
| 2) Resistors- 100 $\Omega$                     | -2  |
| 15 K $\Omega$                                  | -1  |
| 3) Capacitors- 0.01 $\mu$ f                    | -1  |
| 4) TRPS  | -1  |
| 5) CRO   | -1  |
| 6) Bread board CRO probes and connecting wires |     |

**ANALYSIS OF UJT:**

The voltage  $V_{BB}$  is applied between  $B_1$  and  $B_2$ . If  $I_E=0$ , then voltage drop across  $R_{B1}$  is given by,

$$V_{1=} \frac{RB1}{RB1 + RB2} \times V_{BB}$$

The ratio  $\frac{RB1}{RB1+RB2}$  is termed as Intrinsic stand off ratio and is denoted by  $\eta$ .  
 $V_{1=} \eta V_{BB}$

The value of emitter voltage, which makes the diode conduct, is termed as peak voltage and is given by


$$V_p = V_D + V_1$$

$$V_p = V_D + \eta V_{BB}$$


Expression for frequency of oscillation:

$$F = 1/T$$
$$= 1/RC \ln (1/1-\eta)$$

### CIRCUIT DIAGRAM

 

### MODEL GRAPHS:

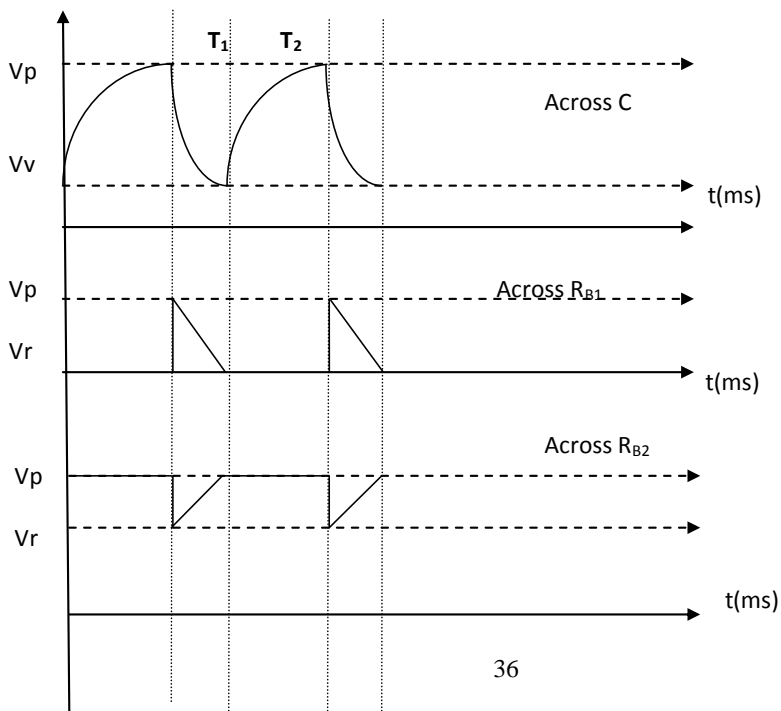

**Observations:**

	Vv	Vp	T <sub>1</sub>	T <sub>2</sub>
Across C				
Across R <sub>B1</sub>				
Across R <sub>B2</sub>				

T<sub>1</sub>----charging time period

T<sub>2</sub> ----discharging time period

F -----frequency of oscillations

$F=1/T$

$F=1/[RC \ln [ (1/(1- \eta))]]$

$\eta =RB1/(RB1+RB2)$

**PROCEDURE:**

1. The circuit is connected as per the circuit diagram.
2. A supply of  $V_{BB}=12v$  is applied to the circuit with the help of TRPS.
3. The output waveforms across capacitor, resistor R<sub>B1</sub> and resistor R<sub>B2</sub> are obtained from the CRO.
4. The frequency of the corresponding signals is noted and the waveforms are plotted on the graph sheet.

**PRECAUTIONS:**

- 1) Loose and wrong connections must be avoided.
- 2) Parallax error should be avoided while taking the readings.

**Conclusion:****RESULT:****Viva questions**

1. What do mean by Intrinsic standoff ratio?
2. Why the wave form of RB2 is getting negative spikes?
3. What is meant by base bias resistor?

**EXPERIMENT: 8**  
**ASTABLE MULTIVIBRATOR USING 555 IC**


**AIM:**

To obtain a symmetric square wave output by maintaining certain duty cycle by using 555 IC.


**APPARATUS:**

- 1) 555 IC
- 2) Resistors 3.3 K $\Omega$
- 3) Capacitors 0.1 $\mu$ F, 0.01 $\mu$ F
- 4) 10K $\Omega$  Potentiometer
- 5) TRPS
- 6) Diode 1N4007 1
- 7)CRO and CRO Probes


**CIRCUIT DIAGRAM:**

 


**PIN DIAGRAM:**

 

555 IC Timer Block Diagram

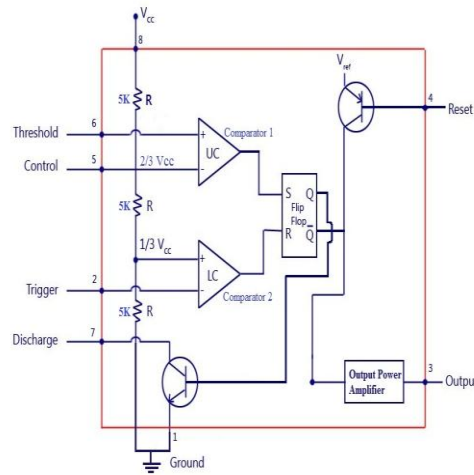

**MODEL GRAPHS:**

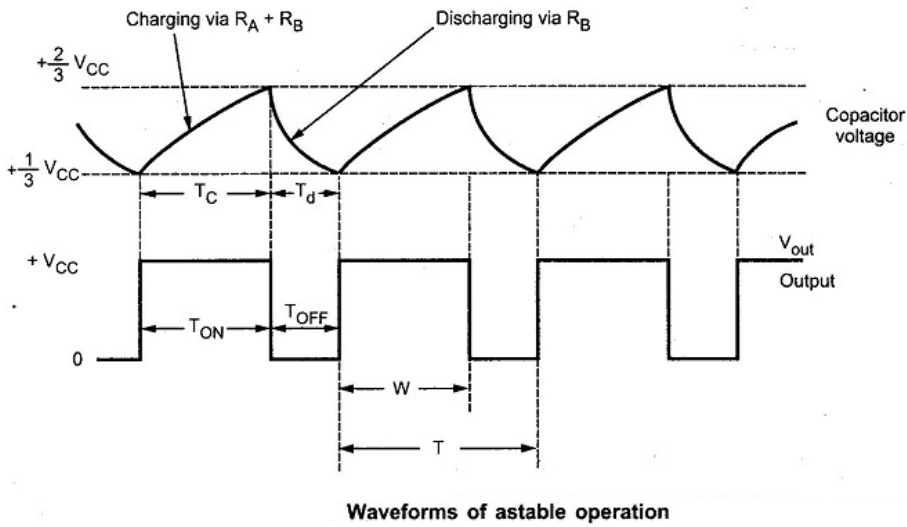

**Duty cycle:** The capacitor voltage for a low pass RC circuit subjected to a step input of  $V_{cc}$  volts is given by

$$V_c = V_{cc} (1 - \exp(-t/RC))$$

The time  $t_1$  taken by the circuit to charge from 0 to  $2/3 V_{cc}$  is,

$$2/3 V_{cc} = V_{cc} (1 - \exp(-t_1/RC))$$

$$t_1 = 1.09 RC$$

The time  $t_2$  to charge from 0 to  $1/3 V_{cc}$  is,

$$1/3 V_{cc} = V_{cc} (1 - \exp(-t_2/RC))$$

$$t_2 = 0.405 RC$$

So the time to charge from  $1/3 V_{cc}$  to  $2/3 V_{cc}$  is

$$t_{HIGH} = t_1 - t_2 = 1.09 RC - 0.405 RC = 0.69 RC$$

So, for the given circuit,

$$t_{HIGH} = 0.69 (R_A + R_B) C$$

The output is low while the capacitor discharges from  $2/3 V_{cc}$  to  $1/3 V_{cc}$  and the voltage across the capacitor is given by

$$1/3 V_{cc} = 2/3 V_{cc} (\exp(-t/RC))$$

$$t_{LOW} = 0.69 RC$$

For the given circuit,  $t_{LOW} = 0.69 R_B C$

Total time period,  $T = t_{HIGH} + t_{LOW} = 0.69 (R_A + 2R_B) C$

Duty cycle =  $t_{HIGH} / T = (R_A + R_B) / (R_A + 2R_B)$

For the modified circuit Duty cycle =  $R_A / (R_A + R_B)$



**PROCEDURE:**

1. The connections are made as per the circuit diagram.
2. Now the potentiometer is adjusted till the 50% duty cycle is achieved. Output waveform is observed on the CRO.
3. Time periods of the output waveform are noted and output waveform is plotted to the scale.
4. The corresponding waveforms for other duty cycles are also obtained and plotted to scale.

Tabular Form:

Duty cycle	$R_A(\Omega)$	$T_{high}$ $\mu$ Sec	$T_{low}$ $\mu$ Sec	Across pinNo:6		Across pin No:3	Frequency Theoretical	Frequency Practical
				$V_1$ (v)	$V_2$ (v)			

**PRECAUTIONS:**

1. Loose and wrong connections should be avoided.
2. Parallax error should be avoided.

**Conclusion:**

**RESULT:**

**Viva questions**

1. What do mean by duty cycle?
2. What is RS flip flop?
3. What is comparator?
4. What are the applications of astable multivibrator?
5. How many stable states we have in astable multivibrator?
6. What is quasi stable state?

**EXPERIMENT: 9**  
**BISTABLE MULTIVIBRATOR**

**AIM:** To design and study the Fixed Bistable multivibrator using transistors.

**APPARATUS:**

- 1) Transistors BC 107 -2
- 2) Resistors 100K $\Omega$  -2  
2.2K $\Omega$  -2  
15k $\Omega$  -2
- 3) Light emitting diodes -2
- 4) Regulated power supply-1
- 5) Bread board and connecting wires
- 6) Digital multi meter (0-20V) -1

**DESIGN OF A BISTABLE MULTIVIBRATOR:**

For the given  $V_{CC}$ ,  $V_{BB}$ ,  $h_{fe (min)}$ ,  $I_{C (sat)}$  it is possible to compute the values of  $R_{C1}$ ,  $R_1$  and  $R_2$ . The following assumptions are made in order to design the bistable fixed bias multivibrator.

1. If  $Q_1$  and  $Q_2$  are identical silicon transistors, the junction voltages are assumed as  $V_{CE (sat)} = 0.3 \text{ V}$  and  $V_{BE (sat)} = 0.7 \text{ V}$ .
2. The base current of the ON transistor is taken as 1.5 times of the minimum value of base current.

$$I_B = 1.5 I_{B (min)}$$

$$\text{Where } I_{B (min)} = I_{C (sat)} / h_{fe (min)}$$

3. The current through  $R_2$  of the ON transistor is taken as one tenth of  $I_C$ .  
If  $Q_2$  ON,  $I_4 = I_{C2}/10$ .
- 4 The current through  $R_1$  is ignored since it is quite small in comparison with the collector current of ON transistor.

**To find  $R_C$ :**

$$R_C = V_{CC} - V_D / I_2 = V_{CC} - V_{CE (sat)} / I_{C (sat)}$$
$$R_{C1} = R_{C2}$$

**To find  $R_2$ :**

The current through  $R_2$  is  $I_4$ , where  $I_4 = I_{C2}/10 = I_{C(sat)}/10$ .

$$R_2 = [V_B - (-V_{BB})] / I_4$$

To find  $R_1$ :

The current through  $R_1$  is  $I'$

$$I' = I_{B2} + I_4$$

$$I_{B2} = 1.5 I_{B(\min)}$$


Where  $I_{B(\min)} = I_{C(\text{sat})} / h_{FE(\min)}$ .

$$I_1 = I'$$

$$I_1 = V_{CC} - V_B / R_{C1} + R_1$$

$$R_1 = [V_{CC} - V_{BE(\text{SAT})} / I_1] - R_{C1}$$

**CIRCUIT DIAGRAM:**

 

**PROCEDURE:**

1. The connections are made as per the circuit diagram.
2. The supply is switched on and it is observed that one LED is ON whereas the other is OFF.
3. Now the base voltages of both the transistors  $V_{B1}$  and  $V_{B2}$  and collector voltages  $V_{C1}$  and  $V_{C2}$  are noted.
4. A negative trigger is given at the base of the ON transistor to change the states of the transistors.
5. In this steady state the base voltages of both the transistors  $V_{B1}$  and  $V_{B2}$  and also the collector voltages  $V_{C1}$  and  $V_{C2}$  are noted.

**PRECAUTIONS:**

1. Loose and wrong connections should be avoided.
2. Parallax error should be avoided.

**Conclusion:****RESULT:****Viva questions**

1. What is stable state?
2. Name the types of multivibrators?
3. What is quasi stable state?
4. How many stable states are there in binary?
5. What is the need of triggering
6. What are the types of triggering are there in multivibrator?

**EXPERIMENT: 10**  
**FREQUENCY RESPONSE OF ACTIVE FILTER**

**AIM:**

To obtain the response of active filters by varying the frequency.

**APPARATUS:**

- 1) OP-AMP LM 741C      -2
- 2) Resistors    10k $\Omega$       -4  
                  16 K $\Omega$       -3
- 3) Capacitors -0.01 $\mu$ f    -3
- 4) Function generator
- 5) TRPS
- 6) CRO & CRO Probes
- 7) Connecting wires & bread board

**THEORY:**

Filters are frequency selective networks, which can allow desired range of frequencies and attenuates other frequencies. Filters are classified:


1. Passive and Active filters
2. Analog and Digital Filters

Depending on the type of the elements used as resistor, capacitor, and inductor such a type of filter is called as passive filters. By using op-amp and transistor on addition to passive elements, they are called as active filters.


Depending on the range of frequencies the active filters can be classified as low pass, band pass, high pass, all pass, band reject filters.

**CIRCUIT DIAGRAM:**


HIGH PASS BUTTERWORTH FILTER

 


### LOW PASS BUTTERWORTH FILTER

 
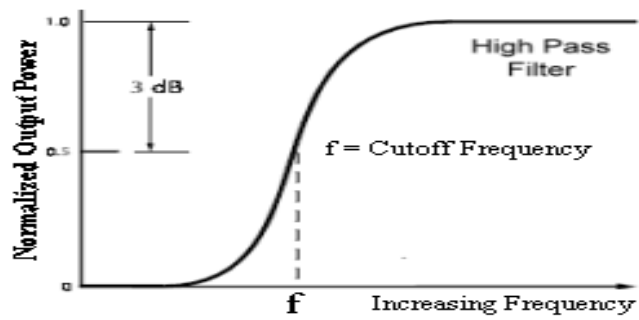
### MODEL GRAPHS: HIGH PASS BUTTERWORTH FILTER



### LOW PASS BUTTERWORTH FILTER

 

**DESIGN:**

**Design of I order Butter worth filter:**

Given the cut off frequency  $F_L$ ,  $A_0$ ,

$$F_L = \frac{1}{2\pi RC}$$

Assume C and then substituting the value in the above formula

Find R, using  $A_0$  and assuming R1 find  $R_F$

**PROCEDURE:**

1. The circuit is connected as per the circuit diagram
2. The Frequency of the input signal is varied and the Corresponding out put voltage is noted. The magnitude of the input Signal is kept constant through out the experiment.
3. The gain for each frequency is calculated using the formula  
Gain in dB =  $20 \log (V_o/V_i)$ .
4. A graph for gain v/s frequency is plotted which is known as Frequency response.

**TABULAR FORM:**

INPUT VOLTAGE: 100 mv (p-p)

**HIGH PASS BUTTERWORTH FILTER**

Frequency (Hz)	Out Put Voltage(V)	Gain= $20\log(V_o/V_i)$ (dB)
100Hz		
to		
1M Hz		

### LOW PASS BUTTERWORTH FILTER

Frequency (Hz)	Out Put Voltage(V)	Gain= $20\log(v_o/v_i)$ (dB)
100Hz to 1M Hz		

#### PRECAUTIONS:

1. Loose and wrong connections should be avoided.
2. Parallax error should be avoided.

#### Conclusion:

#### RESULT:

#### Viva questions

1. What is filter?
2. What is an active filter?
3. What is high pass filters & low pass filters?
4. Name the types of filtes?
5. What is butter worth filter?



**EXPERIMENT: 11**  
**IC OP-AMP BOOT STRAP RAMP GENERATOR**

**AIM:** To generate a ramp wave forms by maintaining constant current conditions by using a boot strap ramp generator with an op-amp 741IC as voltage follower.

**APPARATUS:**

1. Diode 1N4007 - 1
2. Op-amp: LM 741C -1
3. Capacitors --33kpf -1  
0.02μf -1  
2.2 μf -1
4. Resistors - 47kΩ, 470kΩ, 10kΩ
5. Transistors-BC107
6. Function Generator.
7. TRPS
8. Bread Board & Connecting Wires
9. CRO & CRO Probes

**DESIGN:**

For a given  
Maximum diode current is  $I_R = 3\mu A$   
Allowing 1% non linearity due to  $I_R$   
 $I_1 = 100 I_R$   
 $C_1 = I_1 \text{ ( Ramp time/} V_p \text{)}$   
Assume  $V_p = 8V$   
 $V_{R1} = V_{CC} - V_{D1} - V_{CE (sat)}$   
 $R_1 = V_{R1} / I_1$


**For 1% non-linearity due to  $C_3$  discharge:**

$V_{C3} = V_{CC}$   
 $\Delta V_3 = 1\% \text{ of } V_{CC}$   
 $C_3$  discharges current  $I_1$   
 $C_3 = I_1 \text{ ( t / } \Delta V_3 \text{)}$


**Calculation of  $C_2$ :**

Minimum  $I_c$  of  $Q_1 = 10 I_1$   
 $I_B = I_C / h_{fe}$   
 $I = V_{CC} - V_1 / R_B$  where  $R_B = V_{CC} - V_{BE} / I_B$   
 $C_2 = I \text{ ( t / } \Delta V \text{)}$


CIRCUIT DIAGRAM  $V_{CC}(+15V)$

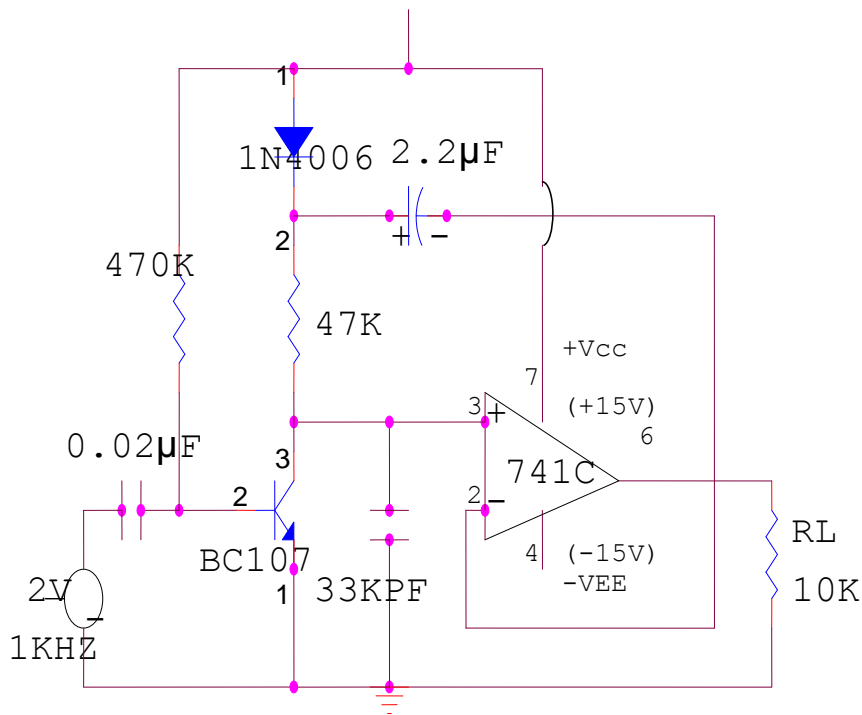

**PIN DIAGRAM**

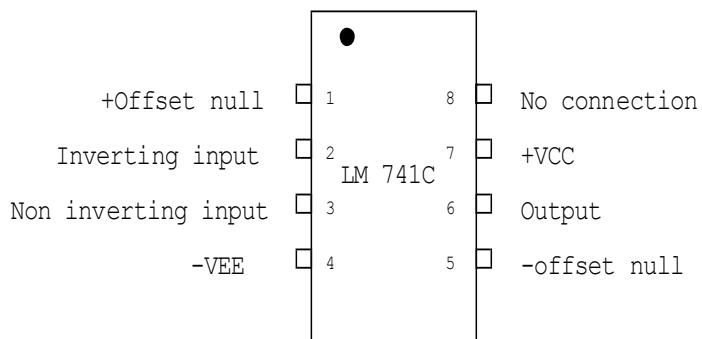

**MODEL GRAPHS:**

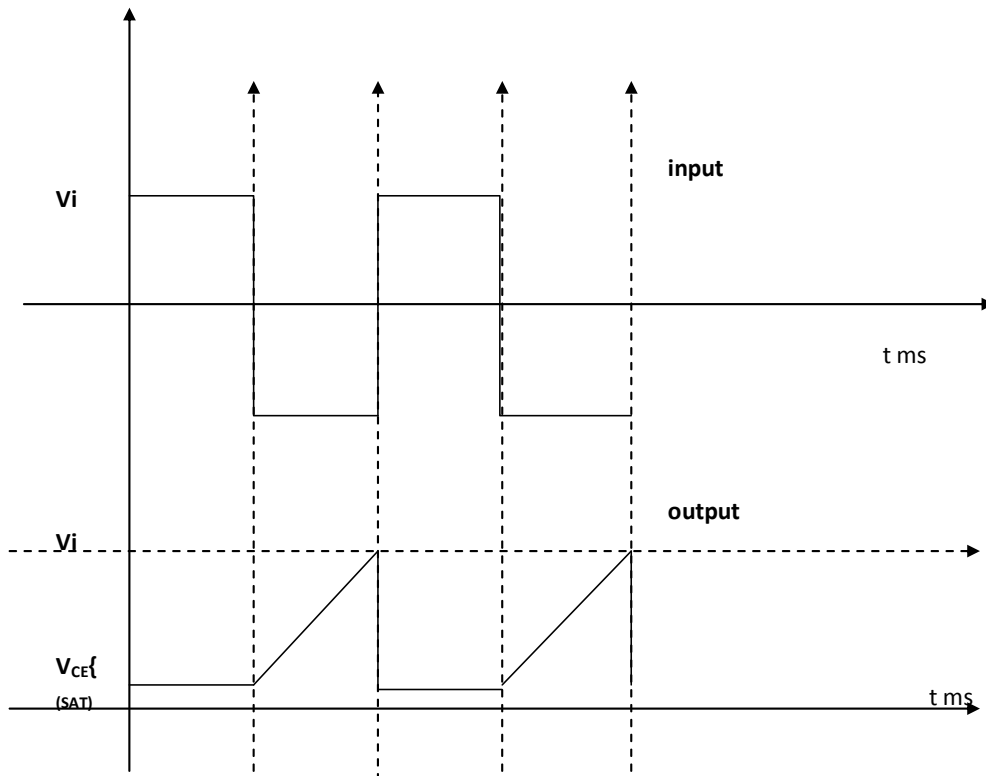

**PROCEDURE:**

1. The circuit is connected as per the circuit diagram.
2. A square wave of 2V (p-p), 1 KHz is applied with the help of function generator to the base of a transistor.
3. The corresponding input and output waveforms are noted from the CRO
4. The graphs are plotted for the input and output waveforms.

**OBSERVATION** $V_{CE} =$ Output Voltage  $V_o =$ Sweep time  $T_s =$ **PRECAUTIONS:**

1. Loose and wrong connections should be avoided.
2. Parallax error should be avoided.

**RESULT:****Viva questions**

1. What is sweep circuit?
2. How the Op-amp acts as a emitter follower?
3. How the current constant is maintained in Boot strap?
4. Name different types of ramp generator?

**MAJOR EQUIPMENT IN  
LINEAR IC'S & PULSES CIRCUITS LABORATORY**

<b>S.NO</b>	<b>DESCRIPTION</b>	<b>MAKE</b>	<b>QUANTITY</b>
1.	20 MHz DUAL TRACE OSCILLOSCOPE	AP LAB /SCIENTIFIC	21
	20 MHz DIGITAL STORAGE OSCILLOSCOPE	FALCON	
2.	1 MHz FUNCTION GENERATOR WITH DIGITAL DISPLAY	AP LAB/ PACIFIC	18
3.	TRPS 0-30V, 2A DUAL CHANNEL	ITL/PACIFIC /FALCON	20
4.	DC MICRO & MILLI AMMETERS	MECO/HI- Q/AQUILA	46
5.	DC MICRO VOLTMETER	MECO/HI- Q/AQUILA	18

<b>6.</b>	<b>BENCH TOP DIGITAL MULTIMETER</b>	<b>METRAVI/ MECO</b>	<b>15</b>
<b>7.</b>	<b>5KVA SERVO CONTROLLED STABILIZER</b>	<b>ITL</b>	<b>01</b>

**TOTAL EXPENDITURE OF LABORATORY: Rs: 6,30,679.71/-**